

Carry Lookahead Adder (2A)

-
-

Copyright (c) 2025 - 2013 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Carry Kill, Propagate, Generate conditions (1)

X	Y		
0	0	K	Kill ($=\bar{P}\bar{G}$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 


<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

 Carry Kill, Propagate, Generate conditions (2)




C₀ propagation condition

 

$$s = p_3 \wedge p_2 \wedge p_1 \wedge p_0$$


$$= (a_3 \oplus b_3) \wedge (a_2 \oplus b_2) \wedge (a_1 \oplus b_1) \wedge (a_0 \oplus b_0)$$

 c_0 can be propagated to c_{out}
only if $s = 1$




https://en.wikipedia.org/wiki/Carry-skip_adder

A FA in terms of **p** and **g**

 

Half Adder	
$S = a \oplus b$	
$C = a \wedge b$	


a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full adder with additional generate and propagate signals.


https://en.wikipedia.org/wiki/Carry-skip_adder

Carry Equations in a Ripple Carry Adder

 

https://en.wikipedia.org/wiki/Carry-skip_adder

A 4-bit Ripple Carry Adder

 

Half Adder 1

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

Half Adder 2

$$c_{i+1} = g_i + p_i \wedge c_i$$

$$s_i = p_i \oplus c_i$$

Critical Path : $c_4 - c_3 - c_2 - c_1 - c_0$: 8 gate delay

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

Expanding carry equations

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0 \quad \rightarrow \quad c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 c_1 \quad \rightarrow \quad c_2 = g_1 + p_1 [g_0 + p_0 c_0]$$

$$c_3 = g_2 + p_2 c_2 \quad \rightarrow \quad c_3 = g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]$$

$$c_4 = g_3 + p_3 c_3 \quad \rightarrow \quad c_4 = g_3 + p_3 [g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]]$$


c_{out}

c_{in}

 


$$\begin{aligned} g_0 + p_0 c_0 &= c_1 \\ g_1 + p_1 g_0 + p_1 p_0 c_0 &= c_2 \\ g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 &= c_3 \\ g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 &= c_4 \end{aligned}$$

 Carry Generate and Carry Propagate Signals



 
*these carries can
be computed in parallel*



Carry equations into Gates (1)

$$c_{i+1} = g_i + p_i c_i$$
 
$$c_4 = g_3 + p_3 [g_2 + p_2 [g_1 + p_1 [g_0 + p_0 c_0]]]$$



8 gate delay

Fan-in number: small
Stage number: large

Ripple Carry Adder

Carry equations into Gates (2)


$g_3 +$
$p_3 g_2 +$
$p_3 p_2 g_1 +$
$p_3 p_2 p_1 g_0 +$
$p_3 p_2 p_1 p_0 c_0$

$$g_0 + p_0 c_0 = c_1$$


$$g_1 + p_1 g_0 + p_1 p_0 c_0 = c_2$$

$$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 = c_3$$

 
$$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 = c_4$$



Sum of Product :
2 gate delay

 


Fan-in number: large
Stage number: small

 


Carry Lookahead Adder

Carry Lookahead Adder

 


Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Carry Lookahead Adder

 

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Replicating carry circuits (1)

 

Half Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$


Half Adder

$$C_{i+1} = g_i + p_i \wedge C_i$$

$$S_i = p_i \oplus C_i$$

*no merit
in reducing
a critical path delay*




Replicating carry circuits (2)

 

*Sum of Product :
2 gate delay*

*c_i 's can be computed
in parallel*

   *since g_i 's and p_i 's
are computed in parallel*



Limitations of Carry Lookahead


AND ₂ , OR ₂		$g_0 + p_0 c_0 = c_1$
AND ₃ , OR ₃		$g_1 + p_1 g_0 + p_1 p_0 c_0 = c_2$
AND ₄ , OR ₄		$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 = c_3$
AND ₅ , OR ₅		$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 = c_4$
⋮	⋮	
AND ₃₂ , OR ₃₂	possible?	$= c_{31}$
AND ₃₃ , OR ₃₃	possible?	$= c_{32}$

Large number of fan-in : impractical




{ High Radix Addition (2^9)
 Multi-level Carry Lookahead





A 4-bit Carry Lookahead Adder

 


A 16-bit adder using four 4-bit CLA's

 

    partition a 16-bit adder into four 4-bit **CLA** blocks : B3, B2, B1, B0



Block CLA Structures (1)

 

Block CLA Structures (2)


Each block computes 4 **g**'s and 4 **p**'s in parallel

As soon as c_{in} , 4 **g**'s, and 4 **p**'s of each block is available,
each block computes 4 carries in parallel


As soon as 4 carries and 4 **p**'s of each block is available,
each block computes 4 sums in parallel

However,
only after c_{out} of B0/B1/B2 is available,
the four carries of B1/B2/B3 can be computed

 These can be computed in parallel,
if block carry generate signal G_{Bi}
and block carry propagate signal P_{Bi}
are used




Multi-level CLA

 

Block Carry Equations

 Let us focus on the carry circuits of each block




Define block G and block P signal to compute c_{16} , c_{12} , c_8 , c_4 in parallel

G_{Bi} denotes the carries
which are generated in the block Bi

$P_{Bi}c_{in}$ denotes the input carry c_{in}
which is propagated through the block Bi

 Block Carry Generate and Propagate Signals



Expanding Block Carry Equations

$$C_{4 \cdot (i+1)} = G_{Bi} + P_{Bi} C_{4 \cdot i}$$

$$C_4 = G_{B0} + P_{B0} C_0 \quad \rightarrow \quad C_4 = G_{B0} + P_{B0} C_0$$


$$C_8 = G_{B1} + P_{B1} C_4 \quad \rightarrow \quad C_8 = G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]$$

$$C_{12} = G_{B2} + P_{B2} C_8 \quad \rightarrow \quad C_{12} = G_{B2} + P_{B2} [G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]]$$

$$C_{16} = G_{B3} + P_{B3} C_{12} \quad \rightarrow \quad C_{16} = G_{B3} + P_{B3} [G_{B2} + P_{B2} [G_{B1} + P_{B1} [G_{B0} + P_{B0} C_0]]]$$


C_{out}

C_{in}

 


$$\begin{aligned} G_{B0} + P_{B0} C_0 &= C_4 \\ G_{B1} + P_{B1} G_{B0} + P_{B1} P_{B0} C_0 &= C_8 \\ G_{B2} + P_{B2} G_{B1} + P_{B2} P_{B1} G_{B0} + P_{B2} P_{B1} P_{B0} C_0 &= C_{12} \\ G_{B3} + P_{B3} G_{B2} + P_{B3} P_{B2} G_{B1} + P_{B3} P_{B2} P_{B1} G_{B0} + P_{B3} P_{B2} P_{B1} P_{B0} C_0 &= C_{16} \end{aligned}$$

Block Carry Generating Circuits

 

Carry Lookahead Logic Comparison

$$C_{i+1} = g_i + p_i C_i$$

 

Block B0 Carries


$$g_0 + p_0 C_0 = C_1$$

$$g_1 + p_1 g_0 + p_1 p_0 C_0 = C_2$$

$$g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0 = C_3$$

$$g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0 = C_4$$
 
$$C_{4 \cdot (i+1)} = G_{Bi} + P_{Bi} C_{4 \cdot i}$$



Group G0 Carries

$$G_{B0} + P_{B0} C_0 = C_4$$

$$G_{B1} + P_{B1} G_{B0} + P_{B1} P_{B0} C_0 = C_8$$


$$G_{B2} + P_{B2} G_{B1} + P_{B2} P_{B1} G_{B0} + P_{B2} P_{B1} P_{B0} C_0 = C_{12}$$

$$G_{B3} + P_{B3} G_{B2} + P_{B3} P_{B2} G_{B1} + P_{B3} P_{B2} P_{B1} G_{B0} + P_{B3} P_{B2} P_{B1} P_{B0} C_0 = C_{16}$$

the same structure

Block Carry Generating Circuits – simplified

 
Let us focus on the carry circuits of each block



has the same structure as the structure of each block

$$\begin{aligned}
 G_{B0} + P_{B0}c_0 &= c_4 \\
 G_{B1} + P_{B1}G_{B0} + P_{B1}P_{B0}c_0 &= c_8 \\
 G_{B2} + P_{B2}G_{B1} + P_{B2}P_{B1}G_{B0} + P_{B2}P_{B1}P_{B0}c_0 &= c_{12} \\
 G_{B3} + P_{B3}G_{B2} + P_{B3}P_{B2}G_{B1} + P_{B3}P_{B2}P_{B1}G_{B0} + P_{B3}P_{B2}P_{B1}P_{B0}c_0 &= c_{16}
 \end{aligned}$$

 G_{B0}, P_{B0} : Block Carry Generate and Propagate




$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$



$$P_{B0} = p_3 p_2 p_1 p_0$$

$$c_4 = G_{B0} + P_{B0} c_0$$

 


G_{B0} denotes the generated carries in the block B0

  $P_{B0} c_0$ denotes the the propagated input carry c_0



 G_{B1}, P_{B1} : Block Carry Generate and Propagate




$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 + p_7 p_6 p_5 p_4 c_4$$

$$G_{B1} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$


$$P_{B1} = p_7 p_6 p_5 p_4$$

$$c_8 = G_{B1} + P_{B1} c_4$$

 


G_{B1} denotes the generated carries in the block B1


 
$P_{B1} c_4$ denotes the the propagated input carry c_4



 G_{B2}, P_{B2} : Block Carry Generate and Propagate



  G_{B3}, P_{B3} : Block Carry Generate and Propagate




$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} + p_{15}p_{14}p_{13}p_{12}c_{12}$$

$$G_{B3} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$

$$P_{B3} = p_{15}p_{14}p_{13}p_{12}$$


$$c_{16} = G_{B3} + P_{B3}c_{12}$$

 


G_{B3} denotes the generated carries in the block B3

$P_{B2}c_8$ denotes the the propagated input carry c_8

 
Block Carry Generating Circuits – detailed




Simple Carry Lookahead Adder – B0

 


Simple Carry Lookahead Adder – B1

 


Simple Carry Lookahead Adder – B2

 


Simple Carry Lookahead Adder – B3

 

 A 2-Level Carry Lookahead Adder – Level 1



Delay calculations of 2-Level CLA (1)

 

Delay calculations of 2-Level CLA (2)

Starting at time of zero:

- calculation of p_i and g_i is done at time 1,
- calculation of the P_{Bi} is done at time 2,
- calculation of the G_{Bi} is done at time 3,
- calculation of the inputs for the $CGen_{Bi}$ from the $CGen_{G0}$ are done at:
 - time 0 for $CGen_{B0}$,
 - time 5 for $CGen_{B1}$, $CGen_{B2}$, $CGen_{B3}$,
- calculation of the S_i are done at:
 - time 4 for Sum_{B0} ,
 - time 8 for Sum_{B1} , Sum_{B2} , Sum_{B3} ,
- calculation of the final carry bit (C_{16}) is done at time 5.

The maximal time is 8 gate delays (for $S_{[4:15]}$).


https://en.wikipedia.org/wiki/Carry-lookahead_adder

A Variation of 2 Level CLA

Ripple Carry Adder + Carry Lookahead

S. & D. Harris, Digital Design and Computer Architecture 2nd ed.

Block Carry Generators

 

block carry generators	block carry in	block carry out
	C_{out}	C_{in}
CG_{B0}	C_4	C_0
CG_{B1}	C_8	C_4
CG_{B2}	C_{12}	C_8
CG_{B3}	C_{16}	C_{12}

A simplified carry lookahead circuit


*computes block carry output much faster
than a ripple carry adder block does*

*Whereas the traditional carry lookahead adder
computes all the carries,*

*the simplified carry lookahead circuit
computes only the block carry output*

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

 A 16-bit adder using four 4-bit Simplified CLA's (1)




B_3, B_2, B_1, B_0 : 4-bit ripple carry adder blocks

$CG_{B_3}, CG_{B_2}, CG_{B_1}, CG_{B_0}$: 4-bit block carry generators

C_{16}, C_{12}, C_8, C_4 : block carries

 
A 16-bit adder using four 4-bit Simplified CLA's (2)



As soon as the block carry input c_{in} and g_i 's and p_i 's are available, a carry lookahead operation can be performed in parallel with a ripple carry adder operation

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

A 4-bit Ripple Carry Adder Block B0

 

when g_i 's and p_i 's are available,
the critical path : $c_4 \leftarrow c_3 \leftarrow c_2 \leftarrow c_1 \leftarrow c_0$: 8 gate delay


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

Two ways of computing a block carry (1)

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

Method 1 : using multiple 2-input gates
 
$$c_4 = g_3 + p_3(g_2 + p_2(g_1 + p_1(g_0 + p_0 c_0)))$$



In a ripple carry adder,
to compute sum bits S_3, S_2, S_1, S_0 ,
carry bits c_4, c_3, c_2, c_1 must be computed

Method 2 : using multi-input gates

$$c_4 = G_{B0} + P_{B0} c_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{B0} = p_3 p_2 p_1 p_0$$


As g_i 's and p_i 's are computed in parallel,
 G_{B0} and P_{B0} can be computed in parallel

the path from c_0 to c_4 is much smaller,
compared to the 1st method

Two ways of computing a block carry (2)

Method 1 : using multiple 2-input gates

$$c_4 = g_3 + p_3(g_2 + p_2(g_1 + p_1(g_0 + p_0 c_0)))$$

 


Method 2 : using multi-input gates

$$c_4 = G_{B0} + P_{B0} c_0$$


$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{B0} = p_3 p_2 p_1 p_0$$

 


A Ripple Carry Adder Block and a Block Carry Generator

a ripple carry adder block

 

Method 1 : using multiple 2-input gates
 
$$c_4 = g_3 + p_3(g_2 + p_2(g_1 + p_1(g_0 + p_0 c_0)))$$



a block carry generator

Method 2 : using multi-input gates

$$c_4 = G_{B0} + P_{B0} c_0$$


$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{B0} = p_3 p_2 p_1 p_0$$


After all g_i 's and p_i 's are available

The longest path : the path from c_{in} to c_{out} : 8Δ

 the carry path
in a ripple carry adder block



a carry lookahead
circuit

 


after g_i 's and p_i 's are available,
it takes 6Δ to compute G_{B0}
And 1Δ delay to compute P_{B0}

the longest path : the path from g_0 to c_{out} : 7Δ

the shortest path : the path from c_{in} to c_{out} : 2Δ

Δ = a gate delay

 After all G_{Bi} 's and P_{Bi} 's are available



after (6+1) Δ , G_{B0} is available.

after (1+1) Δ , P_{B0} is available.


When G_{B0} is available and thus P_{B0} is available,

the longest path : the path from C_{in} ($= C_0$) to C_{out} ($= C_4$) : 2 Δ

the path from P_{B0} to C_{out} ($= C_4$) : 2 Δ

the shortest path : the path from G_{B0} to C_{out} ($= C_4$) : 1 Δ

Block Carry Generator B0

 


a block carry generator B0

$$C_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$

$$G_{B0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{B0} = p_3 p_2 p_1 p_0$$

 

$$C_4 = G_{B0} + P_{B0} C_0$$

$$G_{B0} \leftarrow g_0 : 6\Delta$$

$$G_{B0} \leftarrow g_1 : 5\Delta$$

$$G_{B0} \leftarrow g_2 : 3\Delta$$

$$G_{B0} \leftarrow g_3 : 1\Delta$$

$$G_{B0} \leftarrow p_1 : 6\Delta$$

$$G_{B0} \leftarrow p_2 : 4\Delta$$

$$G_{B0} \leftarrow p_3 : 2\Delta$$

$$P_{B0} \leftarrow p_0 : 1\Delta$$

$$P_{B0} \leftarrow p_1 : 1\Delta$$

$$P_{B0} \leftarrow p_2 : 1\Delta$$

$$P_{B0} \leftarrow p_3 : 1\Delta$$

$$\text{delay}(c_4 \leftarrow g_i) \leq 7\Delta$$

$$\text{delay}(c_4 \leftarrow p_i) \leq 7\Delta$$


$$\text{delay}(c_4 \leftarrow c_0) = 2\Delta$$

$$\text{delay}(G_{B0} \leftarrow g_i) \leq 6\Delta$$

$$\text{delay}(G_{B0} \leftarrow p_i) \leq 6\Delta$$

$$\text{delay}(P_{B0} \leftarrow p_i) = 1\Delta$$

Block Carry Generator B1

 


a block carry generator B1

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 + p_7 p_6 p_5 p_4 c_4$$

$$G_{B1} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

$$P_{B1} = p_7 p_6 p_5 p_4$$

 

$$c_8 = G_{B1} + P_{B1} c_4$$

$$G_{B1} \leftarrow g_7 : 6\Delta$$

$$G_{B1} \leftarrow g_6 : 5\Delta$$

$$G_{B1} \leftarrow g_5 : 3\Delta$$

$$G_{B1} \leftarrow g_4 : 1\Delta$$

$$G_{B1} \leftarrow p_5 : 6\Delta$$

$$G_{B1} \leftarrow p_6 : 4\Delta$$

$$G_{B1} \leftarrow p_7 : 2\Delta$$

$$P_{B1} \leftarrow p_4 : 1\Delta$$

$$P_{B1} \leftarrow p_5 : 1\Delta$$

$$P_{B1} \leftarrow p_6 : 1\Delta$$

$$P_{B1} \leftarrow p_7 : 1\Delta$$

$$\text{delay}(c_8 \leftarrow g_i) \leq 7\Delta$$

$$\text{delay}(c_8 \leftarrow p_i) \leq 7\Delta$$


$$\text{delay}(c_8 \leftarrow c_4) = 2\Delta$$

$$\text{delay}(G_{B1} \leftarrow g_i) \leq 6\Delta$$


$$\text{delay}(G_{B1} \leftarrow p_i) \leq 6\Delta$$

$$\text{delay}(P_{B1} \leftarrow p_i) = 1\Delta$$

Block Carry Generator B2

 

a block carry generator B2

 

$$c_{12} = g_{11} + p_{11} g_{10} + p_{11} p_{10} g_9 + p_{11} p_{10} p_9 g_8 + p_{11} p_{10} p_9 p_8 c_8$$

$$G_{B2} = g_{11} + p_{11} g_{10} + p_{11} p_{10} g_9 + p_{11} p_{10} p_9 g_8$$


$$P_{B2} = p_{11} p_{10} p_9 p_8$$

$$c_{12} = G_{B2} + P_{B2} c_8$$


$G_{B2} \leftarrow g_{11} : 6\Delta$		$P_{B2} \leftarrow p_8 : 1\Delta$
$G_{B2} \leftarrow g_{10} : 5\Delta$	$G_{B2} \leftarrow p_9 : 6\Delta$	$P_{B2} \leftarrow p_9 : 1\Delta$
$G_{B2} \leftarrow g_9 : 3\Delta$	$G_{B2} \leftarrow p_{10} : 4\Delta$	$P_{B2} \leftarrow p_{10} : 1\Delta$
$G_{B2} \leftarrow g_8 : 1\Delta$	$G_{B2} \leftarrow p_{11} : 2\Delta$	$P_{B2} \leftarrow p_{11} : 1\Delta$

$\text{delay}(c_{12} \leftarrow g_i) \leq 7\Delta$	$\text{delay}(G_{B2} \leftarrow g_i) \leq 6\Delta$
$\text{delay}(c_{12} \leftarrow p_i) \leq 7\Delta$	$\text{delay}(G_{B2} \leftarrow p_i) \leq 6\Delta$
$\text{delay}(c_{12} \leftarrow c_8) = 2\Delta$	$\text{delay}(P_{B2} \leftarrow p_i) = 1\Delta$

Block Carry Generator B3

 

a block carry generator B3

 

$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} + p_{15}p_{14}p_{13}p_{12}c_{12}$$

$$G_{B3} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$


$$P_{B3} = p_{15}p_{14}p_{13}p_{12}$$

$$c_{16} = G_{B3} + P_{B3}c_{12}$$

$G_{B3} \leftarrow g_{15} : 6\Delta$		$P_{B3} \leftarrow p_{12} : 1\Delta$
$G_{B3} \leftarrow g_{14} : 5\Delta$	$G_{B3} \leftarrow p_{13} : 6\Delta$	$P_{B3} \leftarrow p_{13} : 1\Delta$
$G_{B3} \leftarrow g_{13} : 3\Delta$	$G_{B3} \leftarrow p_{14} : 4\Delta$	$P_{B3} \leftarrow p_{14} : 1\Delta$
$G_{B3} \leftarrow g_{12} : 1\Delta$	$G_{B3} \leftarrow p_{15} : 2\Delta$	$P_{B3} \leftarrow p_{15} : 1\Delta$

$\text{delay}(c_{16} \leftarrow g_i) \leq 7\Delta$	$\text{delay}(G_{B3} \leftarrow g_i) \leq 6\Delta$
$\text{delay}(c_{16} \leftarrow p_i) \leq 7\Delta$	$\text{delay}(G_{B3} \leftarrow p_i) \leq 6\Delta$
$\text{delay}(c_{16} \leftarrow c_{12}) = 2\Delta$	$\text{delay}(P_{B3} \leftarrow p_i) = 1\Delta$


 
All P_{Bi} 's and all G_{Bi} 's are computed in parallel



$$\begin{aligned} \text{delay}(p_i, g_i \leftarrow a_i, b_i) &= 1\Delta \\ \text{delay}(G_{Bi} \leftarrow p_i, g_i) &\leq 6\Delta \\ \text{delay}(P_{Bi} \leftarrow p_i, g_i) &= 1\Delta \end{aligned}$$



  
$$\begin{aligned} \text{delay}(G_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) &\leq 7\Delta \\ \text{delay}(P_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) &= 2\Delta \end{aligned}$$




from a_i, b_i to G_{Bi}, P_{Bi} : all in $(1+6)\Delta$

Delay to generate all G_{Bi} and P_{Bi} : $(1+6)\Delta$

 
from a_i, b_i to G_{Bi}, P_{Bi} : all in $(1+6)\Delta$



 
from a_i, b_i to G_{Bi}, P_{Bi} : all in $(1+6)\Delta$



 from a_i, b_i to G_{Bi}, P_{Bi} : all in $(1+6)\Delta$



 from a_i, b_i to G_{Bi}, P_{Bi} : all in $(1+6)\Delta$



$$\begin{aligned} \text{delay}(p_i, g_i \leftarrow a_i, b_i) &= 1\Delta \\ \text{delay}(G_{Bi} \leftarrow p_i, g_i) &\leq 6\Delta \\ \text{delay}(P_{Bi} \leftarrow p_i, g_i) &= 1\Delta \end{aligned}$$



$$\begin{aligned} \text{delay}(G_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) &\leq 7\Delta \\ \text{delay}(P_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) &= 2\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(c_o \leftarrow G_{Bi}) &= 1\Delta \\ \text{delay}(c_o \leftarrow P_{Bi}) &= 2\Delta \\ \text{delay}(c_o \leftarrow c_i) &= 2\Delta \end{aligned}$$




$$\begin{aligned} \text{delay}(c_o \leftarrow G_{Bi} \leftarrow a_i, b_i) &\leq 8\Delta \\ \text{delay}(c_o \leftarrow P_{Bi} \leftarrow a_i, b_i) &= 4\Delta \\ \text{delay}(c_o \leftarrow c_i) &= 2\Delta \end{aligned}$$


p_i, g_i : all computed in parallel

Block carries are computed sequentially

 
can compute c_{16}
after c_{12} , G_{B3} and P_{B3} are available



 
can compute c_{12}
after c_8 , G_{B2} and P_{B2} are available



 can compute c_8
after c_4 , G_{B1} and P_{B1} are available



 can compute c_4
after c_0 , G_{B0} and P_{B0} are available



to compute block carries,
 G_{Bi} and P_{Bi} must be available

after 7Δ ,
 G_{Bi} and P_{Bi} must be available


Block Carry Dependencies

$C_0 \rightarrow C_4 \rightarrow C_8 \rightarrow C_{12} \rightarrow C_{16}$


$$\text{delay}(G_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) \leq 7\Delta$$

$$\text{delay}(P_{Bi} \leftarrow p_i, g_i \leftarrow a_i, b_i) = 2\Delta$$

 
The critical path for block carries after 7Δ



 
Parallel computations for each block carry input



 the critical path =
three carry lookahead paths +
the last ripple carry adder block path




 Delays to generate all block carries c_4, c_8, c_{12}, c_{16}




last block carry generator is not necessary

 Delay from $c_{4 \cdot (i-1)}$ to $c_{4 \cdot i} : 2\Delta$, after 7Δ









 The last block carry generator is not needed





*only a ripple carry adder is deployed
without a carry lookahead circuit*


to trade off between speed and area

      

  Computing $S_{i+3}, S_{i+2}, S_{i+1}, S_i$ for a block carry input c_i



 Delays to sum bits S_0, S_1, S_2, S_3 from block carry input c_0



$$\begin{aligned} \text{delay}(S_0 \leftarrow c_0) &= 1\Delta \\ \text{delay}(S_1 \leftarrow c_1) &= 1\Delta \\ \text{delay}(S_2 \leftarrow c_2) &= 1\Delta \\ \text{delay}(S_3 \leftarrow c_3) &= 1\Delta \end{aligned}$$

from internal carries
to sum bits

+

$$\begin{aligned} \text{delay}(c_1 \leftarrow c_0) &= 2\Delta \\ \text{delay}(c_2 \leftarrow c_1) &= 2\Delta \\ \text{delay}(c_3 \leftarrow c_2) &= 2\Delta \end{aligned}$$

from block carry inputs
to internal carries




$$\begin{aligned} \text{delay}(S_0 \leftarrow c_0) &= 1\Delta \\ \text{delay}(S_1 \leftarrow c_0) &= 3\Delta \\ \text{delay}(S_2 \leftarrow c_0) &= 5\Delta \\ \text{delay}(S_3 \leftarrow c_0) &= 7\Delta \end{aligned}$$

from block carry inputs
to sum bits


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

Delays for the last block

 

$$\text{delay}(c_{16} \leftarrow c_{12}) = k T_{FA} = 4 \cdot 2 \cdot \Delta$$

 $k T_{FA}$ = the carry path delay
in a k -bit ripple carry adder block



$$\text{delay}(S_{15} \leftarrow c_{12}) = k T_{FA} - 1 = 7 \cdot \Delta$$


Unless multi-level carry lookahead methods are used,
in the last block, only a ripple carry adder is deployed
without a carry lookahead circuit

to trade off between speed and area


carries c_{15} , c_{14} , c_{13} needs to be computed
for sum bits S_{15} , S_{14} , S_{13} , S_{12}

the carry lookahead circuit does not help much
in the last block

 
$$\text{delay}(c_{16} \leftarrow c_{12}) = T_{ANDOR} = 2 \cdot \Delta$$



Delays to sum bits and internal carries

 

 Delays to sum bits from block carry inputs



T_{pg} , T_{pg_block}

T_{pg} : path delay from a_i, b_i to p_i, g_i 1Δ


T_{pg_block} : path delay from p_i, g_i to G_{Bi}, P_{Bi} 6Δ

$T_{pg} + T_{pg_block}$: path delay from a_i, b_i to G_{Bi}, P_{Bi} 7Δ

after $T_{pg} + T_{pg_block}$, all G_{bi} 's, P_{bi} 's are available.

But each carry lookahead circuit can compute its own c_{out} , only after c_{in} is ready.

 
Thus, $c_0 \rightarrow c_4 \rightarrow c_8 \rightarrow c_{12}$ forms a critical path, after all G_{Bi} and P_{Bi} are computed (7Δ)



	$C_{in} \rightarrow C_{out}$	<i>Lookahead circuits</i>		<i>Ripple Carry Adder</i>
in the 1 st block,	$C_0 \rightarrow C_4$	$T_{AND_OR} = 2\Delta$	$C_0 \rightarrow C_4$	$k \cdot T_{FA} = 4 \cdot 2 \Delta = 8\Delta$
in the 2 nd block,	$C_4 \rightarrow C_8$	$T_{AND_OR} = 2\Delta$	$C_4 \rightarrow C_8$	$k \cdot T_{FA} = 4 \cdot 2 \Delta = 8\Delta$
in the 3 rd block,	$C_8 \rightarrow C_{12}$	$T_{AND_OR} = 2\Delta$	$C_8 \rightarrow C_{12}$	$k \cdot T_{FA} = 4 \cdot 2 \Delta = 8\Delta$
in the 4 th block,	$C_{12} \rightarrow C_{16}$	$T_{AND_OR} = 2\Delta$	$C_{12} \rightarrow C_{15}$	$k \cdot T_{FA} = 4 \cdot 2 \Delta = 8\Delta$
	$C_0 \rightarrow C_{out}$	<i>Lookahead circuits</i>	$C_0 \rightarrow C_{out}$	<i>Ripple Carry Adder</i>
in the 1 st block,	$C_0 \rightarrow C_4$	$1 \cdot T_{AND_OR} = 2\Delta$	$C_0 \rightarrow C_4$	$1 \cdot k \cdot T_{FA} = 1 \cdot 4 \cdot 2 \Delta = 8\Delta$
in the 2 nd block,	$C_0 \rightarrow C_8$	$2 \cdot T_{AND_OR} = 4\Delta$	$C_0 \rightarrow C_8$	$2 \cdot k \cdot T_{FA} = 2 \cdot 4 \cdot 2 \Delta = 16\Delta$
in the 3 rd block,	$C_0 \rightarrow C_{12}$	$3 \cdot T_{AND_OR} = 6\Delta$	$C_0 \rightarrow C_{12}$	$3 \cdot k \cdot T_{FA} = 3 \cdot 4 \cdot 2 \Delta = 24\Delta$
in the 4 th block,	$C_0 \rightarrow C_{16}$	$4 \cdot T_{AND_OR} = 8\Delta$	$C_0 \rightarrow C_{15}$	$4 \cdot k \cdot T_{FA} = 4 \cdot 4 \cdot 2 \Delta = 32\Delta$

from $c_{4 \cdot (i-1)}$ to $c_{4 \cdot i} : 2 \Delta$

$$T_{AND_OR} = 2\Delta$$

 

Delays for each block carry input c_0, c_4, c_8, c_{12}

While carry lookahead operation is performed,
the sum bits are computed by a ripple carry adder



when c_0 is available after $T_{pg} + T_{pg_block} + 0 \cdot T_{AND_OR}$
the 1st block's ripple carry adder and
the 1st blocks carry lookahead circuits can compute in parallel

when c_4 is available after $T_{pg} + T_{pg_block} + 1 \cdot T_{AND_OR}$
the 2nd block's ripple carry adder and
the 2nd blocks carry lookahead circuits can compute in parallel

when c_8 is available after $T_{pg} + T_{pg_block} + 2 \cdot T_{AND_OR}$
the 3rd block's ripple carry adder and
the 3rd blocks carry lookahead circuits can compute in parallel


when c_{12} is available after $T_{pg} + T_{pg_block} + 3 \cdot T_{AND_OR}$
the 4th block's ripple carry adder and
the 4th blocks carry lookahead circuits can compute in parallel

a ripple carry adder

  

a carry lookahead circuit

$$T_{AND_OR}^*(N/k-1)$$

 


$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow G_{Bi}) &= 1\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow B_{Bi}) &= 2\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(G_{Bi} \leftarrow a_i, b_i) &\leq 7\Delta \\ \text{delay}(B_{Bi} \leftarrow a_i, b_i) &= 2\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &\leq 8\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &= 4\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2\Delta \end{aligned}$$

computed in serial

$$kT_{FA} + T_{AND_OR}^*(N/k-1)$$

 


$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow G_{Bi}) &= 1\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow B_{Bi}) &= 2\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(G_{Bi} \leftarrow a_i, b_i) &\leq 7\Delta \\ \text{delay}(B_{Bi} \leftarrow a_i, b_i) &= 2\Delta \end{aligned}$$

$$\begin{aligned} \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &\leq 8\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow a_i, b_i) &= 4\Delta \\ \text{delay}(c_{4(i+1)} \leftarrow c_{4i}) &= 2\Delta \end{aligned}$$

computed in serial
 
$$T_{pg} + T_{pg_block} + T_{AND_OR} * (N/k - 1) + kT_{FA}$$



Multi-input vs. multiple 2-input gates (1)

multi-input NAND gates vs. multiple 2-input NAND

a trade-off between transistor count, area, and speed, as well as design library availability.

While a multi-input NAND gate uses

+ fewer transistors

(N PMOS and N NMOS for an N-input gate)

+ a simpler structure,

– slower fall times and

– larger overall transistor sizes.

Conversely, using multiple 2-input NAND gates

– slower overall speed and

– increased area.

Google AI Overview : vlsi 2-input nand vs multi-input nand


Multi-input vs. multiple 2-input gates (2)

Structure:

An N -input NAND gate requires N parallel PMOS transistors for the pull-up network and N series NMOS transistors for the pull-down network.

Benefits:

 Reduced Transistors: Uses fewer transistors compared to cascading 2-input NANDs for the same logic function.



Drawbacks:

Slower Fall Time:

increasing pull-down resistance with more inputs, slowing down the output's transition to a LOW state.

Larger Transistor Sizes:

wider PMOS transistors to maintain drive strength, which can increase the physical area of the gate.

Library Limitations: Standard VLSI cell libraries may not provide multi-input NAND gates with fan-ins greater than 4 or 5, limiting their practical use

when compared to 2-input NAND gate



Google AI Overview : vlsi 2-input nand vs multi-input nand


Multi-input vs. multiple 2-input gates (3)

Multi-input NAND:

where area and transistor count are critical, and where the performance impact of slower fall times is acceptable.

One 4-input NAND:

4 p-type transistors
4 n-type transistors
Total 8 transistors

 


Multiple 2-input NANDs:

when speed (fast fall time) is a priority, or when designing with standard cell libraries that lack large fan-in gates.



Three 2-input NAND

 3 * 2 p-type transistors
3 * 2 n-type transistors
Total 12 transistors



Google AI Overview : vlsi 2-input nand vs multi-input nand

Multi-input vs. multiple 2-input gates (4)

  	multi-input		2-input
			
area	A_m	$>$	A_2
fall time	Δ_m	$>$	Δ_2
			
area	A_m	$<$	$3 \cdot A_2$
propagation delay	Δ_m	$<$	$3 \cdot \Delta_2$

larger fall time per gate,
but smaller propagation delay in total
similarly, larger area per gate,
but smaller area in total

Google AI Overview : vlsi 2-input nand vs multi-input nand

Unequal rise and fall times (1)

interconnect mismatches and unbalanced drivers

- *unequal rise and fall times,*
- *signal integrity issues*

- *glitches*
- *delay faults*
- *increased power dissipation*
- *logic malfunctions*
- *reduced circuit reliability.*

*These asymmetries create
unbalanced parasitic effects,
causing signals to propagate at different speeds
and potentially corrupting the intended logic,
especially in high-frequency, high-density chips.*

Google AI Overview : vlsi unequal fall and rise times cause serious problems or not

Unequal rise and fall times (2)

Crosstalk and Noise:

unbalanced drivers and

different interconnect lengths

- *unequal parasitic capacitance and inductance*
- *increased crosstalk.*
- *unintended voltage pulses (glitches) or signal delays.*

Signal Delay Faults:

unequal transition times

- *crosstalk and signal skew*
- *delay faults,*
signals arrive at their destination later than expected
 - *particularly detrimental in high-speed circuits,*

Logic Malfunctions:

The introduced noise pulses or delays

- *can flip the logic value*
 - *incorrect outputs*
 - *logic errors.*

Increased Power Consumption:

mismatched transition times,

during parallel or in-phase switching

- *affect how parasitics are charged / discharged*
- *increased dynamic power dissipation*

Google AI Overview : vlsi unequal fall and rise times cause serious problems or not

Unequal rise and fall times (3)

Why it's a growing problem:

High-Density and High-Frequency Designs:

*as VLSI technology scales down,
chip density increases,
operating frequencies rise.
→ exacerbates parasitic coupling*

Process Variations:

*Random variations in semiconductor fabrication
→ differences in interconnect lengths
and driver strengths
→ unequal rise and fall times.*

*To mitigate these issues, designers employ
techniques to balance transition times, control impedance, and reduce crosstalk,
ensuring reliable operation in modern VLSI circuits.*


Google AI Overview : vlsi unequal fall and rise times cause serious problems or not

Four cases of Method 2

Case A – B	(2-input, 2-input)	6 Δ	3 Δ	6 Δ	+ 1 Δ	= 7 Δ
Case A – B'	(2-input, m-input)	6 Δ	1 Δ	6 Δ	+ 1 Δ	= 7 Δ
Case A' – B	(m-input, 2-input)	2 Δ	3 Δ	3 Δ	+ 1 Δ	= 4 Δ
Case A' – B'	(m-input, m-input)	2 Δ	1 Δ	2 Δ	+ 1 Δ	= 3 Δ

using multiple 2-input gates



 
large propagation delay
small power consumption



In the book of S. & D. Harris's book


using multi-input gates

   small propagation delay
large power consumption




In the book of S. & D. Harris's book

Case 1 (A - B)

 

Case 2 (A - B')

 


p_i, g_i can be computed in parallel


P_{Bj}, G_{Bj} can be computed in parallel
after p_i, g_i are computed

In the book of S. & D. Harris's book

 
Case A - B
Case A - B'
Case A' - B
Case A' - B'




Case 3 (A' - B)

 

Case 4 (A' - B')

 


 Delays to generate all block carries c_4, c_8, c_{12}, c_{16}




	G	P	
Case A – B	7 Δ (2)	4 Δ (1)	7 Δ
Case A – B'	7 Δ (2)	2 Δ (1)	7 Δ
Case A' – B	3 Δ (1)	4 Δ (2)	4 Δ
Case A' – B'	3 Δ (2)	2 Δ (1)	3 Δ


Multi-level Carry Lookahead

 

Contiguous Multi-level Carry Lookahead

 

Carry Skip Adder

 

Any kill or generate condition results in divided (broken) critical paths

All FA's in R-2 groups must have the propagate condition